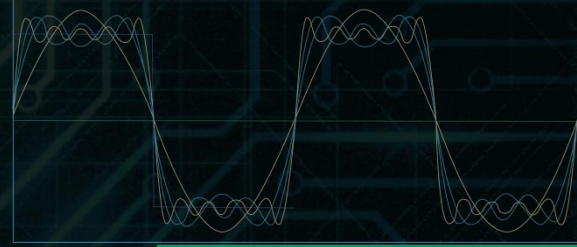




Measurement and



Sensor Technologies






03


Signal Conditioning

Signal conditioning can include amplification, filtering, transformation, conversion, modulation, range matching, isolation and many more processes which may be required to **make sensor output suitable for processing after conditioning.**

3 Signal Conditioning

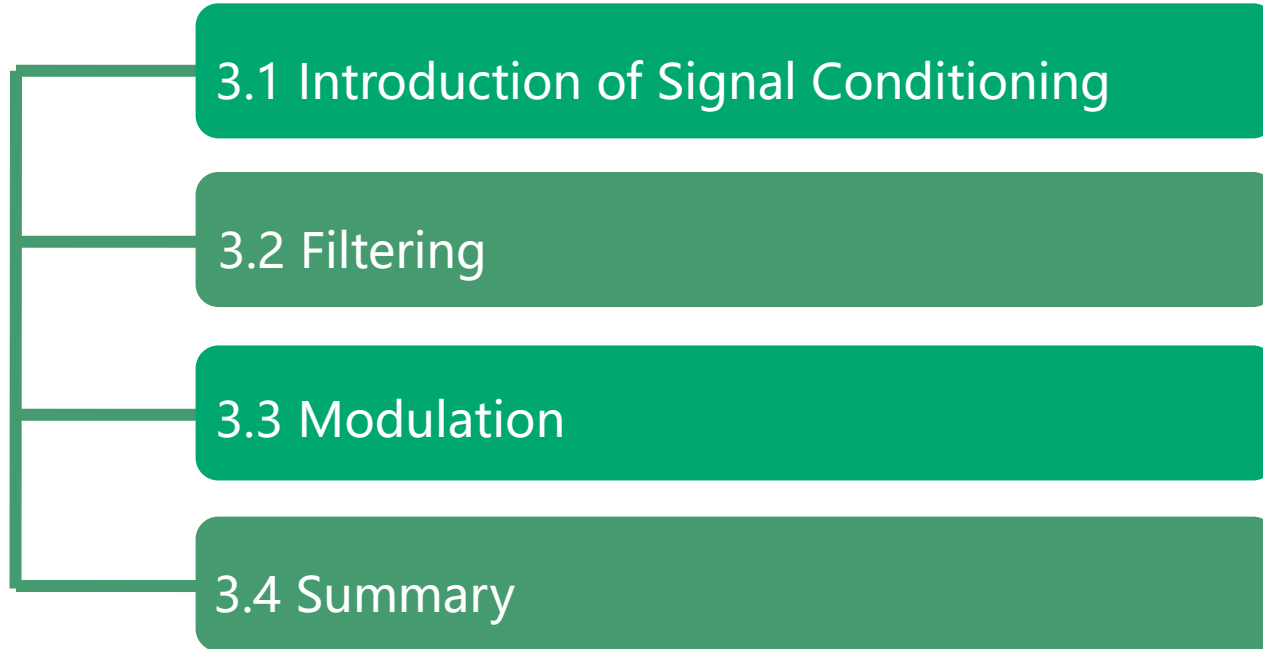

3.1 Introduction of Signal Conditioning

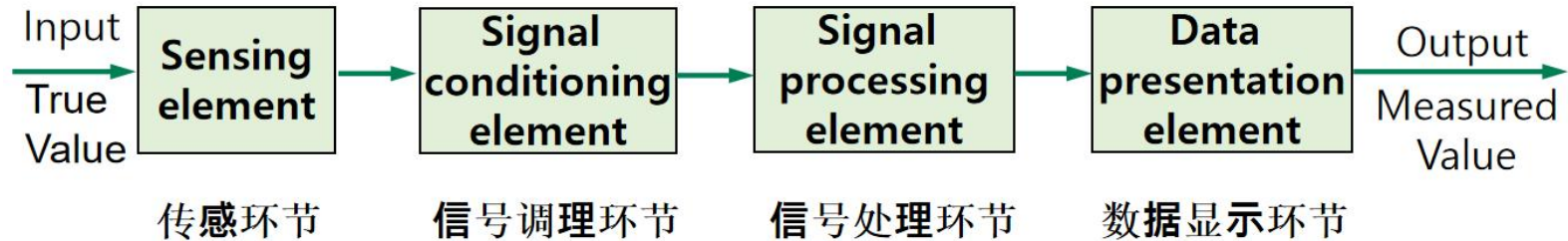

- In the study of electronics, signal conditioning signifies manipulating an analog signal in such a way that it **meets the requirements of the next stage for further processing**.
- Signal conditioning can include **amplification, filtering, transformation, conversion, modulation, range matching, isolation** and many more processes which may be required to make sensor output suitable for processing after conditioning.

3.2 Filtering

1) What the filter does

- A filter is a frequency selection device that **allows certain frequency components in a signal to pass** while greatly **attenuating other frequency components**




- ✓ Pass specific frequency components in the signal
- ✓ Greatly attenuates other frequency components
- Filters out interfering noise or unwanted frequency band signals


3.2 Filtering

2) Types of filter


- The filters are specified based on a **transfer function** $H(j\omega)$ in terms of its **amplitude** $|H(j\omega)|$, **phase** $\angle H(j\omega)$, or delay responses— $|d\angle H(j\omega)/d\omega|$.

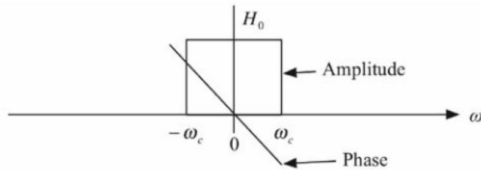


Low-pass

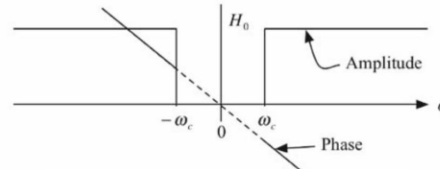

High-pass

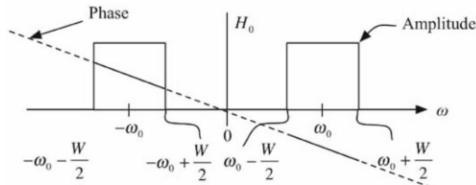

Band-pass

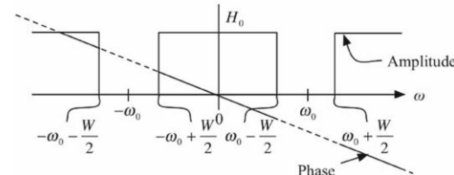

Band elimination

3.2.1 Simple Low-pass Filters



1) The ideal low-pass filter transfer function

■ The words low-pass means that when the signal $x(t)$ is passed through a low-pass filter, only low frequencies, say 0 to $f_c = \omega_c/2\pi$, are passed and block all frequencies above the cutoff frequency f_c .

$$H_{LP}(j\omega) = H_0 \Pi \left[\frac{\omega}{2\omega_c} \right] e^{-j\omega t_0}$$

$$|H_{LP}(j\omega)| = H_0 \Pi \left[\frac{\omega}{2\omega_c} \right] = \begin{cases} H_0 & |\omega| \leq \omega_c \\ 0 & |\omega| \geq \omega_c \end{cases}, \omega_c = 2\pi f_c$$

$$\angle H_{LP}(j\omega) = -\omega t_0$$

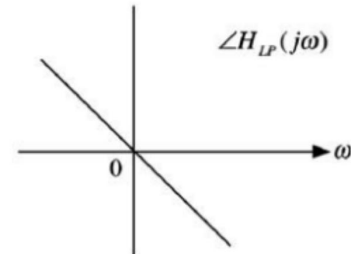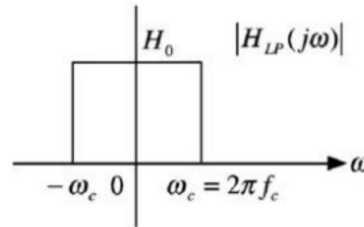


■ The phase response is assumed to be linear, i.e., slope is constant.
The group delay is $t_0 = -\frac{d\angle H_{LP}(j\omega)}{d\omega}$.

3.2.1 Simple Low-pass Filters

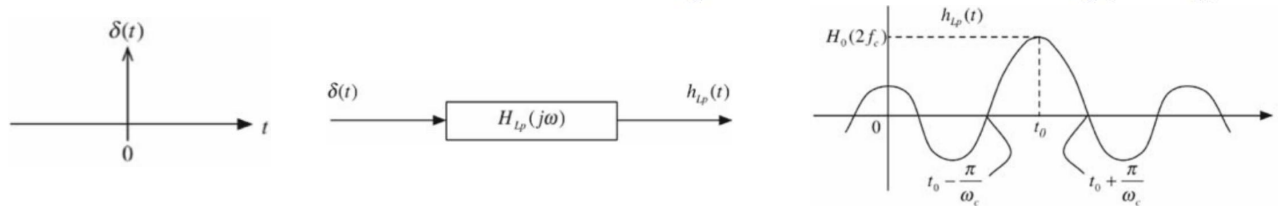2) The impulse response of the ideal low-pass filter

■ For a physically realizable system, the impulse response $h(t) = 0$ for $t < 0$, i.e., the system is causal. For a realizable system, the output cannot exist before the input is applied. The impulse response of the ideal low-pass filter can be determined from below.

$$h_{LP}(t) = F^{-1}[H_{LP}(j\omega)] = F^{-1}\left[H_0 \Pi\left[\frac{\omega}{2\omega_c}\right] e^{-j\omega t_0}\right] = H_0(2f_c) \frac{\sin(\omega_c(t - t_0))}{\omega_c(t - t_0)}$$






■ There is output before the input is applied. The ideal low-pass filter is not causal and is physically unrealizable.

3.2.1 Simple Low-pass Filters

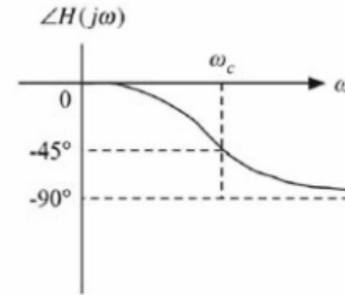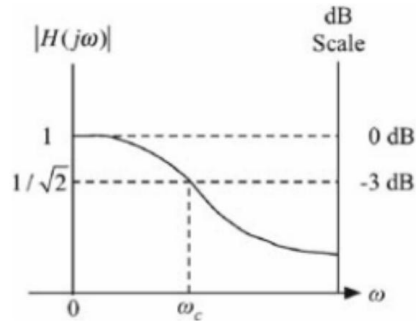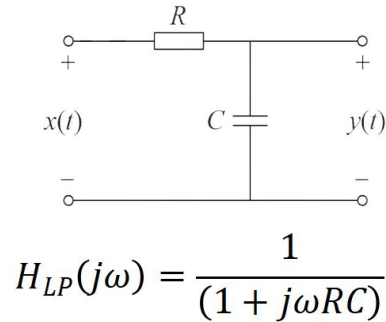3) RC low pass filter

■ The RC filter circuit is simple, and the standard resistance-capacitance components are easily available, so it is often used in the field of engineering testing. The circuit of the RC low-pass filter and its amplitude-frequency and phase-frequency characteristics are shown in the following figure:



■ Cut-off frequency $f_c = f_{3dB} = (1/2\pi RC)$, it is shown that the RC value determines the cutoff frequency of the filter.

3.2.1 Simple Low-pass Filters

Example 3.1

■ Consider the RC circuit shown in Figure 3.6 with the source and the load resistors. Derive the transfer function and sketch the amplitude characteristic function for the two cases. a. $R_L = \infty$ and b. $R_L = R_S$.

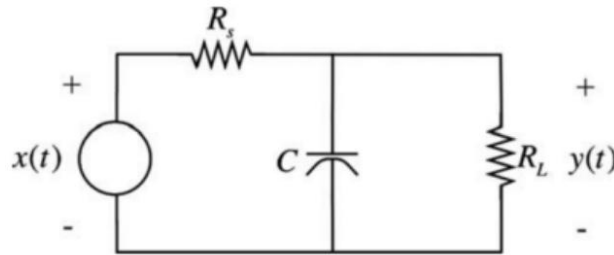


Figure 3.6 Example 3.1

3.2.1 Simple Low-pass Filters

Example 3.1

■ Solution: The transfer functions are given by

$$\left[\frac{Y(s)}{X(s)}\right] = H_{LP}(s) = \frac{Z_2}{Z_2 + Z_1} \quad Z_2 = \frac{R_L/Cs}{R_L + \frac{1}{Cs}} = \frac{R_L}{1 + R_LCs}, \quad Z_1 = R_s$$

$$\left[\frac{Y(s)}{X(s)}\right]_b = H_{LP}(s) = \frac{\frac{R_L}{R_s R_L C}}{s + \left[\frac{R_L + R_s}{R_s R_L C}\right]} = \frac{K}{s + \omega_c} \quad K = \frac{1}{R_s C}, \quad \omega_c = \frac{R_s + R_L}{R_s R_L C}$$

■ In case a, the load resistance is infinite, i.e., the circuit is not loaded. In case b. $R_L = R_s$. For the two cases the corresponding transfer functions are

$$\text{a. } H_{LP, R_L \rightarrow \infty}(s) = \frac{1/R_s C}{s + \frac{1}{R_s C}}$$

$$\text{b. } H_{LP, R_L = R_s}(s) = \frac{1/R_s C}{s + \frac{2}{R_s C}}$$

3.2.1 Simple Low-pass Filters

Example 3.1

$$\text{a. } H_{LP, R_L \rightarrow \infty}(s) = \frac{1/R_s C}{s + \frac{1}{R_s C}} \quad \text{b. } H_{LP, R_L = R_s}(s) = \frac{1/R_s C}{s + \frac{2}{R_s C}}$$


■ In both cases, the gain constant is the same. However, the cutoff frequency is increased in the case of a load resistance. Note that the peak value of the amplitude response function in case b. is $1/2$. So, the 3dB frequency corresponds to the value of the magnitude of the function equal to $(1/2) \times (1/\sqrt{2})$. At $\omega = 0$ the filter circuit is transparent; at $\omega = \infty$ there is no signal transmission; in between these frequencies, the output signal amplitude attenuation is determined by the equation $|Y(j\omega)| = |H(j\omega)||X(j\omega)|$. At the 3dB frequency ω_{3dB} .

$$|Y(j\omega)|_{\omega=\omega_{3dB}} = \frac{1}{\sqrt{2}} |X(j\omega)|_{\omega=\omega_{3dB}}$$

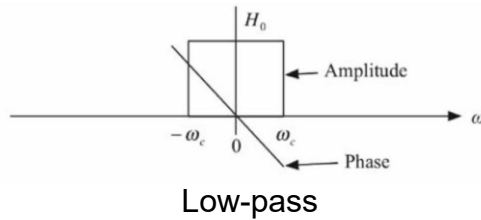3.2.2 Simple High-Pass Filters


Generation from low-pass filtering to high-pass filtering

- In the ideal low- and high-pass filter cases, it can be seen that



$$|H_{LP}(j\omega)|_{\omega=0} = |H_{HP}(j\omega)|_{\omega=\infty} = 1 \text{ and}$$

$$|H_{HP}(j\omega)|_{\omega=0} = |H_{LP}(j\omega)|_{\omega=\infty} = 0$$

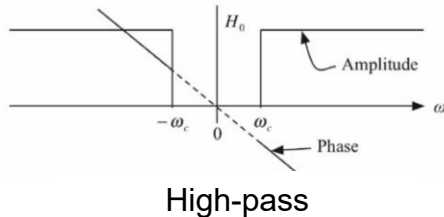

1(low – pass) $\rightarrow$ 0(high – pass) or


0(high – pass) $\rightarrow$ 1(low – pass)

- A logical conclusion is that $\omega \rightarrow 1/\omega$ (i.e., $s \rightarrow 1/s$) provides a transformation that gives a way to find a high-pass filter function from a low-pass filter function.

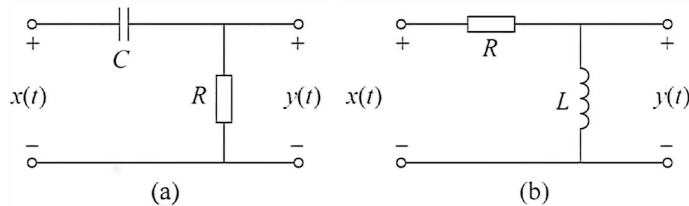3.2.2 Simple High-Pass Filters

Generation from low-pass filtering to high-pass filtering

■ Using the RC and the RL low-pass circuits, we have two simple high-pass filters shown in Figure 3.7 a, b, one is a RL and the other one is a RC circuit.



$$H_{Hpa}(s) = \frac{s}{s + \frac{1}{RC}}, H_{Hpb}(s) = \frac{s}{s + \frac{R}{L}}$$



$$H_{Hpa}(j\omega) = \frac{j\omega}{j\omega + \frac{1}{RC}}, H_{Hpb}(j\omega) = \frac{j\omega}{j\omega + \frac{R}{L}}$$

$$|H_{Hpa}(j\omega)| = \frac{|\omega|}{\sqrt{\omega^2 + (\frac{1}{RC})^2}}$$

$$\angle H_{Hpa}(j\omega) = 90^\circ - \tan^{-1}(\omega RC)$$

$$|H_{Hpb}(j\omega)| = \frac{|\omega|}{\sqrt{\omega^2 + (\frac{R}{L})^2}}$$
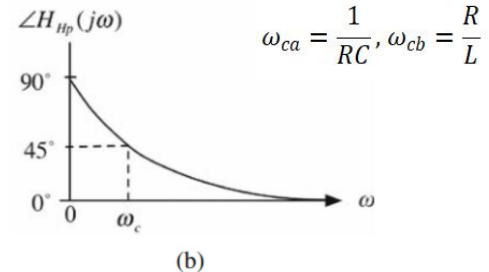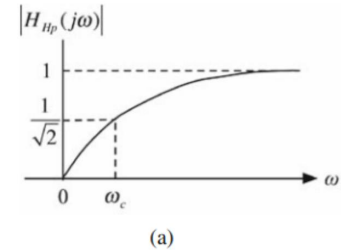
$$\angle H_{Hpb}(j\omega) = 90^\circ - \tan^{-1}\left(\frac{\omega L}{R}\right)$$



3.2.3 Simple Band-Pass Filters

1) Second order transfer function of a bandpass filter

■ A second-order function that has the band-pass characteristics is

$$H_{Bp}(s) = \frac{H_0 a s}{s^2 + a s + b} = \frac{H_0 \frac{\omega_0}{Q} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

- The center frequency $\omega_0 = \sqrt{\omega_{\text{low}} \omega_{\text{high}}}$, ω_{low} and ω_{high} are two cutoff (or 3 dB) frequencies;
 - The 3 dB bandwidth $\beta = \omega_{\text{high}} - \omega_{\text{low}}$;
 - The quality factor $Q = \frac{\omega_0}{\omega_{\text{high}} - \omega_{\text{low}}}$;
- ω_0 is not in the middle of the pass-band. It is the geometric center of the pass-band edges.

■ For simplicity the gain constant is assumed to be $H_0 = 1$ in the following.

The corresponding transfer function, the amplitude, and phase responses are given by



$$H_{Bp}(j\omega) = \frac{(\frac{\omega_0}{Q})j\omega}{\omega_0^2 - \omega^2 + j(\frac{\omega_0}{Q})\omega} = \frac{j}{Q(\frac{\omega_0}{\omega} - \frac{\omega}{\omega_0}) + j}$$
$$|H_{Bp}(j\omega)| = \frac{1}{\sqrt{1 + Q^2(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega})^2}}$$
$$\angle H_{Bp}(j\omega) = \tan^{-1} Q(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega})$$

3.2.3 Simple Band-Pass Filters

1) Second order transfer function of a bandpass filter

$$|H_{Bp}(j\omega)| = \frac{1}{\sqrt{1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}}$$
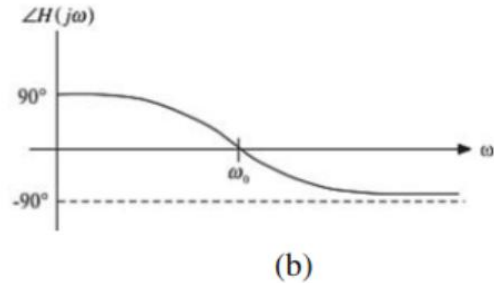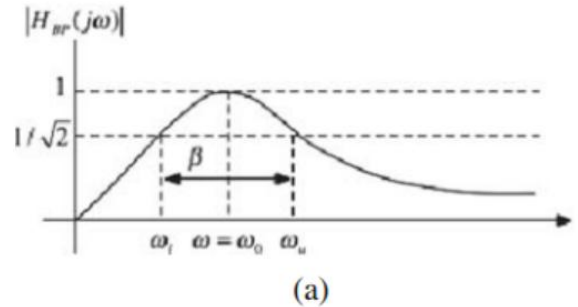
$$\angle H_{Bp}(j\omega) = \tan^{-1} Q \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$



$$|H_{Bp}(j\omega)|^2 \Big|_{\omega=\omega_l, \omega_u} = \frac{1}{2} \rightarrow Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2 = 1 \quad \text{Assuming that } Q > 1/2, \text{ the positive roots are given by } \omega_l, \omega_u = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} \mp \frac{\omega_0}{2Q}$$

$$\beta = \omega_{\text{high}} - \omega_{\text{low}} = \frac{\omega_0}{Q} \quad \omega_0^2 = \omega_l \omega_u \rightarrow \omega_0 = \sqrt{\omega_l \omega_u}$$

The bandwidth decreases as Q increases and vice versa. The filter is assumed to be narrowband if ω_0 is very large compared to the bandwidth of the filter, i.e. As a rough measure, we assume the filter is a narrowband filter if $Q = \frac{\omega_0}{\beta} \geq 10$. For the narrowband case the edges of the pass-band and ω_0 are given below.

$$\omega_l, \omega_u = \omega_0 \mp \frac{\omega_0}{2Q}$$

In this case, ω_0 is in the middle of the 3 dB frequencies and is the center frequency.

3.2.3 Simple Band-Pass Filters

Example 3.2

■ Consider the circuit shown in Figure 3.10. Find the transfer function and derive the expressions for the center frequency, bandwidth, and the quality factor.

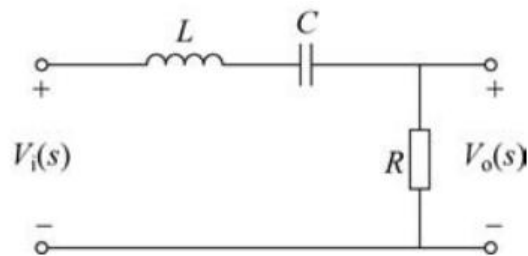


Figure 3.10 A simple band-pass filter

■ Solution: The transfer functions are

$$H_{Bp}(s) = \frac{v_o(s)}{v_i(s)} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \quad |H_{Bp}(j\omega)| = \frac{\frac{R}{L}|\omega|}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\omega \frac{R}{L})^2}}$$
$$H_{Bp}(j\omega) = \frac{\frac{R}{L}j\omega}{\frac{1}{LC} - \omega^2 + j\omega \frac{R}{L}} \quad \angle H_{Bp}(j\omega) = 90^\circ - \tan^{-1} \frac{\frac{R}{L}\omega}{\frac{1}{LC} - \omega^2}$$
$$\omega_0 = \sqrt{\frac{1}{LC}}, \quad \beta = \frac{R}{L} \quad Q = \frac{\omega_0}{B} = \sqrt{\frac{L}{CR^2}}$$

3.2.3 Simple Band-Pass Filters

Example 3.2

■ Also, inductors are never ideal and can be modeled by a resistor in series with an ideal inductor shown in Figure 3.11 resulting in the impedance of the nonideal inductor as $R_i + sL$. The new transfer function and the amplitude response are

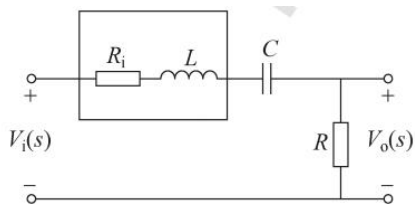


Figure 3.11 A simple band-pass filter with a nonideal inductor

$$H_{Bp}(s) = \frac{\frac{R}{L}s}{s^2 + \frac{R + R_i}{L}s + \frac{1}{LC}}$$

$$|H_{Bp}(j\omega)| = \frac{\frac{R}{L}|\omega|}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + \omega^2 \frac{R_i + R}{L}}}$$


- The center frequency is the same as before.
- The maximum value of the amplitude response is now $R/(R_i + R)$.
- The new bandwidth is $(R_i + R)/L$.
- The Q value is reduced.

Nonideal inductors make the amplitude response less peaked with an increase in the bandwidth, i.e., the amplitude response becomes lower and broader.

3.2.3 Simple Band-Pass Filters

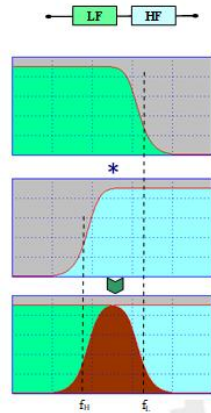
2) Construction of a Bandpass Filter

■ A band-pass filter can be viewed as a cascaded low-pass and a high-pass filter combination with the cutoff frequency of the low-pass filter greater than the cutoff frequency of the high-pass filter, $\omega_{c,Lp} > \omega_{c,Hp}$.




low pass filter

bandpass filter

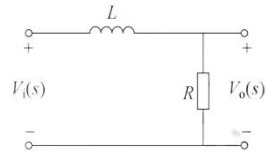


low pass filter


replace L by a series LC circuit

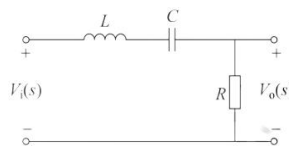

bandpass filter

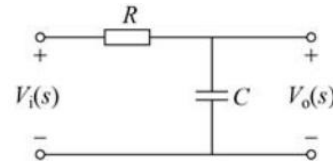

replace C by a parallel LC circuit

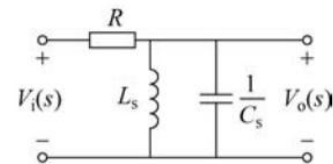

In the two simple low-pass circuits considered earlier, the RL circuit, with the replacement of the inductor by a series LC circuit results in the circuit studied above. By replacing the capacitor in the RC low-pass circuit by a parallel LC circuit results in a band-pass circuit.

3.2.4 Simple Band-Elimination Filters

Second-Order Transfer Function of Band-Stop Filter

- A second-order notch filter has a transfer function of the form

$$H_{Be}(s) = \frac{s^2 + 2bs + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$\lim_{s \rightarrow 0} H_{Be}(s) = 1, \lim_{s \rightarrow \infty} H_{Be}(s) = 1$$

A special and an interesting case is when $b = 0$ and for this case

$$|H_{Be}(j\omega)| \cong \frac{|\omega_0^2 - \omega^2|}{\sqrt{(\omega_0^2 - \omega^2)^2 + \left(\frac{\omega_0}{Q}\omega\right)^2}} \quad \angle H_{Be}(j\omega) = -\tan^{-1} \frac{\frac{\omega_0}{Q}\omega}{\omega_0^2 - \omega^2} \quad |H_{Be}(j\omega)|_{\omega=0} = 1$$



$$\lim_{\omega \rightarrow \infty} |H_{Be}(j\omega)| = 1$$

- The 3 dB frequencies are obtained by equating $|H(\omega_{3dB})| = 1/\sqrt{2}$. The two frequencies are

$$\omega_l, \omega_u = \omega_0 \pm \frac{\omega_0}{2Q}, \beta = \frac{\omega_0}{Q} \quad \text{If } b \neq 0, \text{ then } |H_{Be}(j\omega)|_{\omega=\omega_0} = \frac{Qb}{\omega_0}$$

- The attenuation will be significant at the notch frequency as ω_0 is usually large. Also, note the phase reversal at $\omega = \omega_0$ in the phase response.

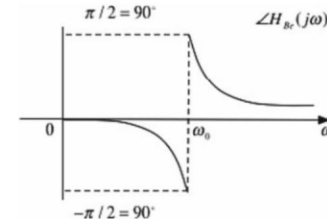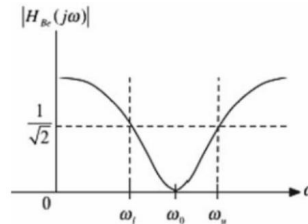Notch filters are used wherever a narrowband of frequencies needs to be eliminated from a received signal.



3.2.4 Simple Band-Elimination Filters

Example 3.3

■ Band-elimination filters can be derived from low-pass filters by replacing an inductor (capacitor) by a parallel LC (series LC) circuit. Consider the circuit in Figure 3.15 with a nonideal inductor with the equivalent impedance of the coil equal to $R_W + j\omega Ls$. Assuming the circuit is not loaded, the output current is zero. Derive the transfer function and show it corresponds to a band-elimination filter.

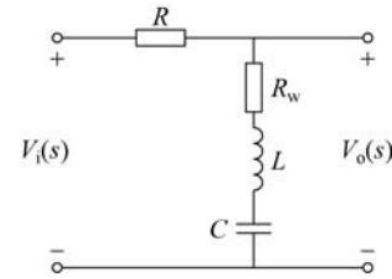


Figure 3.15 A band-elimination filter with a nonideal inductor

3.2.4 Simple Band-Elimination Filters

Example 3.3

■ Solution: The transfer function, its amplitude and phase responses are

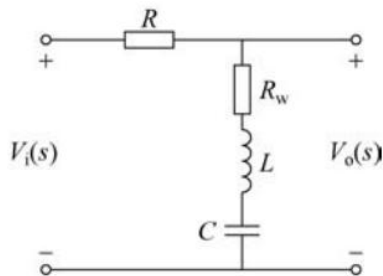


Figure 3.15 A band-elimination filter with a nonideal inductor

$$H_{Be}(s) = \frac{R_w + Ls + \frac{1}{Cs}}{R + R_w + Ls + \frac{1}{Cs}} = \frac{1 + R_ws + LCs^2}{1 + LCs + (R + R_w)Cs}$$

$$|H_{Be}(j\omega)| = \frac{\sqrt{(1 - \omega^2 LC)^2 + (\omega R_w C)^2}}{\sqrt{(1 - \omega^2 LC)^2 + (\omega(R + R_w)C)^2}}$$

$$H_{Be}(j\omega) = \frac{R_w + j\omega L + \frac{1}{j\omega C}}{R + R_w + j\omega L + \frac{1}{j\omega C}} = \frac{1 - \omega^2 LC + j\omega R_w C}{1 - \omega^2 LC + j\omega(R + R_w)C}$$

$$\angle H_{Be}(j\omega) = \tan^{-1} \frac{R_w C \omega}{1 - \omega^2 LC} - \tan^{-1} \frac{\omega(R + R_w)C}{1 - \omega^2 LC}$$


The transfer function has the band-elimination characteristics as

$$\lim_{\omega \rightarrow 0} H_{Be}(j\omega) = 1, \lim_{\omega \rightarrow \infty} |H_{Be}(j\omega)| = 1 \quad \text{and} \quad |H_{Be}(j\omega)|_{\omega = \frac{1}{\sqrt{LC}}} = \frac{R_w}{R + R_w}$$


If the winding resistance R_w is large, then the peak value of the amplitude response is close to 1. we have $2b = R_w/L$, $\omega_0 = 1/\sqrt{LC}$ and $\omega_0/Q = (R + R_w)/L$. The notch bandwidth is $B = |\omega_0/Q| = |(R + R_w)/L|$. In the ideal case, a second-order notch filter can be obtained from a second-order band-pass filter by replacing the parallel (series) LC circuit by a series (parallel) LC circuit.

3.2 Filtering


(a) low pass filter

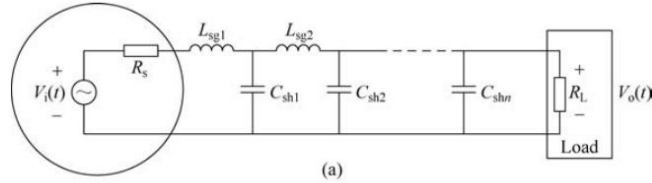

(b) high pass filter

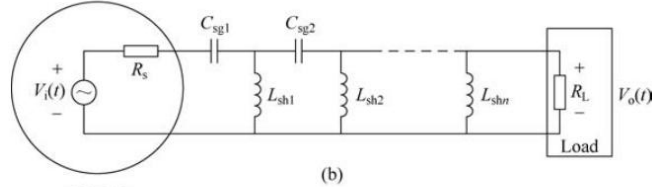

(c) bandpass filter

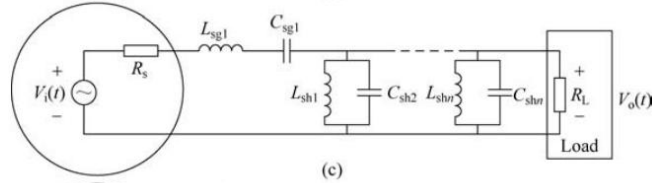

(d) band stop filter

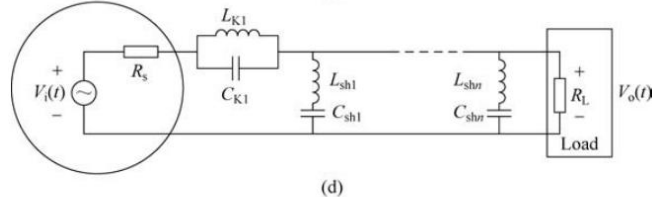


Figure 3.16 Passive filters


3.3 Modulation

1) Purpose of modulation

- To maintain realizable antenna height, to provide the facility of multiplexing and channel separation and to get higher level of noise immunity, a number of modulation schemes are employed both in the case of analog and digital communication.
- Realize the transmission of slowly varying signals, especially over long distances
- Improve anti-jamming capability and signal-to-noise ratio in signal transmission



声音信号

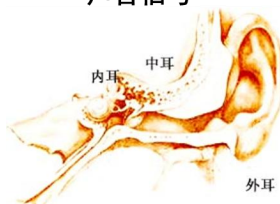

调制
Modulation

解调
Demodulation



广播电台的发射塔

接收





Control a certain parameter (amplitude, frequency or phase) of a high-frequency AC signal (carrier signal) with a slowly varying signal (modulation signal), then AC amplify, transmit, and finally demodulate the amplified signal

3.3 Modulation

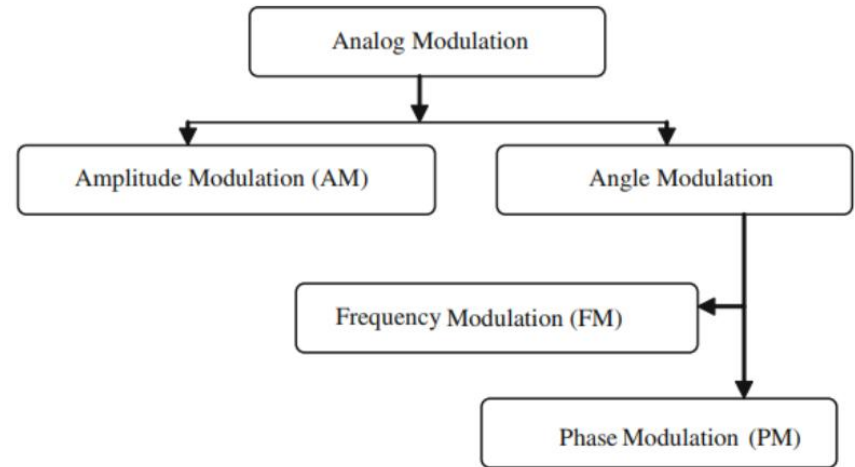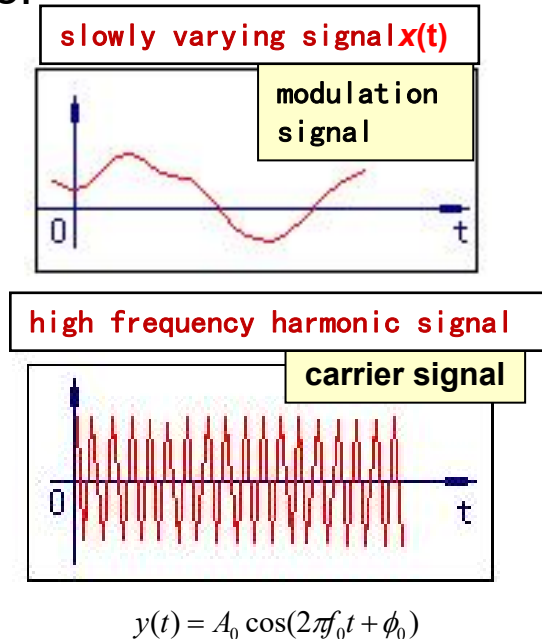2) Types of modulation

- The classification is as shown in Figure.



a) Amplitude Modulation 幅值调制(简称调幅, AM)

b) Frequency Modulation 频率调制(简称调频, FM)

c) Phase Modulation 相位调制(简称调相, PM)

3.31 Amplitude Modulation

1) Modulation Index(AM)

■ The amplitude of the carrier signal is modulated according to the instantaneous amplitude of the modulating signal. In other words change in amplitude, is proportional to the modulating signal $m(t)$. By considering the proportionality constant 1.

$$\Delta \text{amplitud} \propto m(t) \Rightarrow \Delta \text{amplitud} = m(t)$$

■ The modulation index for AM(μ) is inversely proportional to the amplitude of carrier signal(V_c) and directly proportional to the amplitude of modulating signal(V_m).

$$\mu \propto \frac{1}{V_c} \quad , \quad \mu \propto V_m \quad \longrightarrow \quad \mu = \frac{V_m}{V_c}$$

3.31 Amplitude Modulation

2) Math model of AM

■ Modulating signal $m(t) = V_m \sin(\omega_m t)$ and single tone carrier $V_c(t) = V_c \sin(\omega_c t)$ where $\omega_c \gg \omega_m$. Modulated carrier would be

$$\varphi_{AM}(t) = A(t) \sin \omega_c t \quad \text{where,} \quad A(t) = V_c + \Delta \text{amplitud} = V_c + m(t) = V_c + V_m \sin \omega_m t$$

$$\varphi_{AM}(t) = (V_c + V_m \sin \omega_m t) \sin \omega_c t = V_c \sin \omega_c t + \frac{V_m}{2} [\cos(\omega_c - \omega_m)t - \cos(\omega_c + \omega_m)t]$$


$$\varphi_{AM}(t) = V_c \sin \omega_c t + \frac{\mu V_c}{2} \cos(\omega_c - \omega_m)t - \frac{\mu V_c}{2} \cos(\omega_c + \omega_m)t$$

■ The amplitude modulated signal contains three frequency components as f_c , $f_c + f_m$ and $f_c - f_m$. The 2 said frequencies are named as lower and upper side frequency signals. The bandwidth of the single tone AM is $[(f_c + f_m) - (f_c - f_m)] = 2f_m$.


3.31 Amplitude Modulation

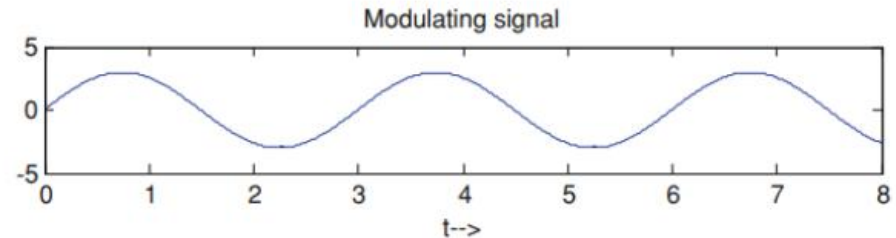2) Math model of AM


modulation signal: $m(t) = V_m \sin \omega_m t$



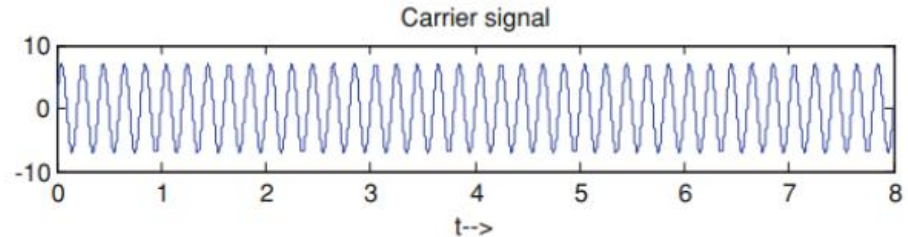carrier signal: $V_c(t) = V_c \sin \omega_c t$



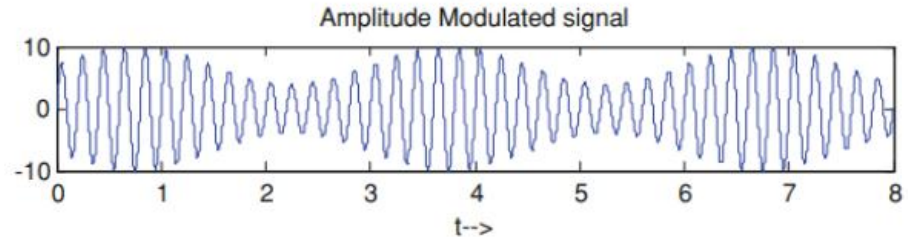amplitude modulation wave: $\varphi_{AM}(t)$



$$\varphi_{AM}(t) = V_c \sin \omega_c t + \frac{\mu V_c}{2} \cos(\omega_c - \omega_m)t - \frac{\mu V_c}{2} \cos(\omega_c + \omega_m)t$$

Figure 3.19 Waveforms Before and After Amplitude Modulation

3.32 Angle Modulation

1) Mathematic Model

■ We can modulate the angle or phase of a signal in two ways. As the angle of a signal is essentially a function of the frequency, we can modulate frequency (FM) or directly modulate the entire angle/phase (PM) to get angle modulation.

FM: Modulating signal $m(t)$ and carrier signal $V_c(t) = A\cos(\omega_c t)$, The frequency after modulation is $\omega_c + \Delta\omega$.

$$\Delta\omega \propto m(t), \Delta\omega = k_f m(t)$$

where k_f is the constant of frequency modulation. Therefore, the instantaneous frequency of carrier after modulation is

$$\begin{aligned}\omega_i &= \omega_c + \Delta\omega = \omega_c + k_f m(t) \\ \theta_i &= \int_{-\infty}^t \omega_i(t) dt = \int_{-\infty}^t [\omega_c + k_f m(t)] dt = \omega_c t + k_f \int_{-\infty}^t m(t) dt\end{aligned}$$

frequency modulation wave: $\varphi_{FM}(t) = A \cos \theta_i(t) = A \cos \left[\omega_c t + k_f \int_{-\infty}^t m(t) dt \right]$


3.32 Angle Modulation

1) Mathematic Model

FM is to use the amplitude of the signal $m(t)$ to modulate the frequency of the carrier, or the FM wave is a constant-amplitude wave with different sparse density that changes with the voltage amplitude of the signal $m(t)$.

frequency
modulation wave:
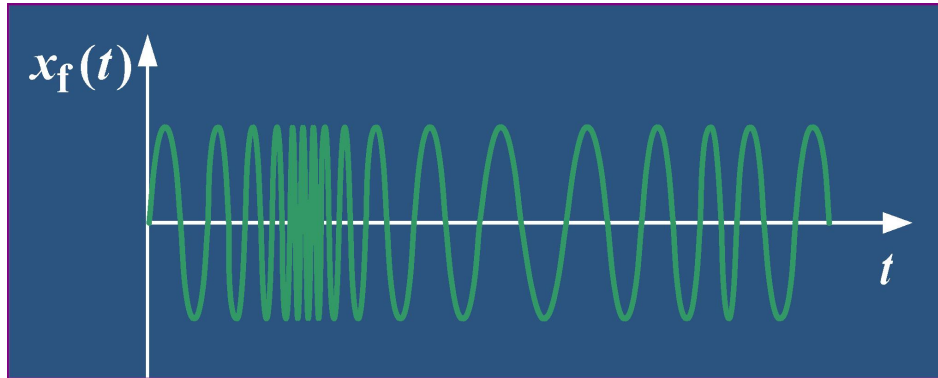
$$\varphi_{FM}(t) = A \cos \theta_i(t) = A \cos \left[\omega_c t + k_f \int_{-\infty}^t m(t) dt \right]$$



FM waves are equal amplitude waveforms that vary in density as the signal changes.

3.32 Angle Modulation

1) Mathematic Model

■ Similarly, if we employ Phase Modulation, the change in angle is directly proportional to the modulating signal.

PM: Modulating signal $m(t)$ and carrier signal $V_c(t) = A\cos(\omega_c t)$, The angle after modulation is $\omega_c t + \Delta\theta$.
 $\Delta\theta \propto m(t)$,

$$\Delta\theta = k_p m(t)$$

where k_f is the constant of phase modulation. Therefore, the instantaneous angle/phase of carrier after modulation is

$$\theta_i = \omega_c t + \Delta\theta = \omega_c t + k_p m(t)$$

$$\omega_i = \frac{d\theta_i(t)}{dt} = \frac{d}{dt}(\omega_c t + k_p m(t)) = \omega_c + k_p \frac{dm(t)}{dt}$$

phase modulation wave: $\varphi_{PM}(t) = A \cos \theta_i(t) = \varphi_{FM}(t) = A \cos [\omega_c t + k_p m(t)]$

3.32 Angle Modulation

2) FM and PM are Interchangeable

■ we can change the entire angle (or phase) of carrier signal either by modifying the frequency or by modifying the phase. That's why PM and FM are the two sub-classes of the broader class of angle modulation. From the mathematical models derived in the previous section, it can also be shown that FM and PM are interchangeable and thereafter inseparable.

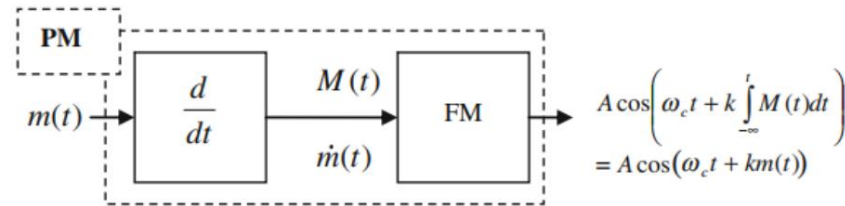


Figure 3.20 FM modulator along with a differentiator used as PM Modulator

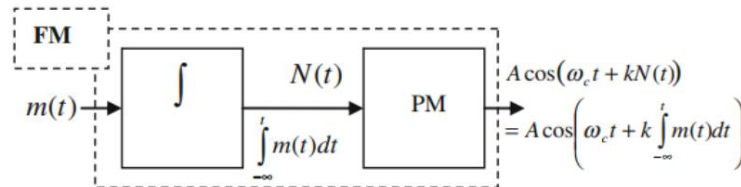


Figure 3.21 PM modulator along with an integrator used as FM modulator

3.4 Summary

- The basic low-pass,high-pass,band-pass,band-elimination filters and the ideal filter functions that describe their functions,and simple circuits that can be used as filters have discussed.
- Analog modulation signifies modification of three basic properties of analog single tone carrier signal according to the analog base band signal.